

Report of Lab 2: More on Static and Dynamic Diode Responses Using OrCAD

Islam Ibrahim - 21010247 - Section 5 - 2026
Department of Electronics and Communication Engineering
Alexandria University

1 1st Circuit



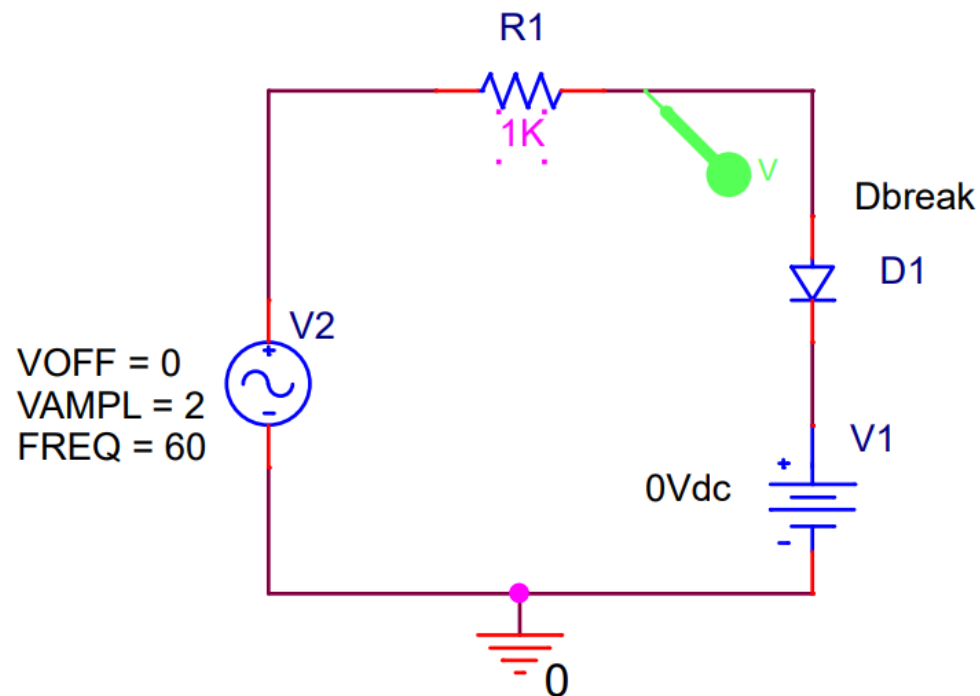


Figure 1: 1st Circuit Simulation

1.1 I_s Change with Time

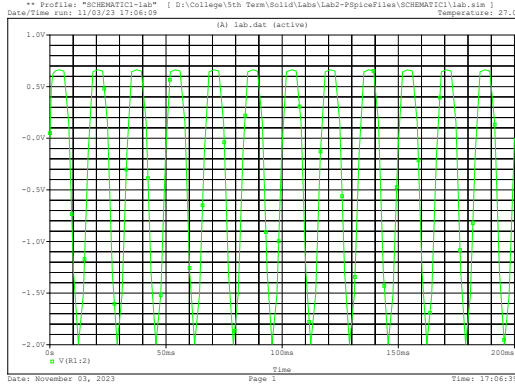

(a) $I_s = 10^{-14} A$

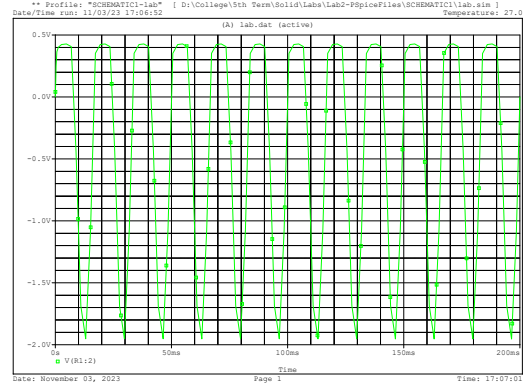


(b) $I_s = 10^{-10} A$

Figure 2: I_s Change with Time Plots


1.1.1 Discussion

Analyze the results obtained we understand that more I_s value gives higher peak to peak voltage amount on the output as relation $V_D = NV_t \ln(\frac{I_d}{I_s} + 1)$ so I_s indirect proportional with V_D .

1.2 N Change with Time

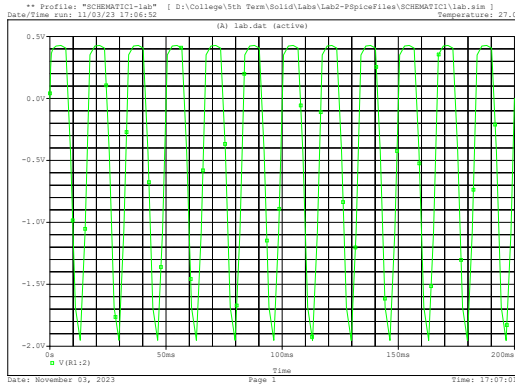

(a) $I_s = 10^{-10} A, N = 1$

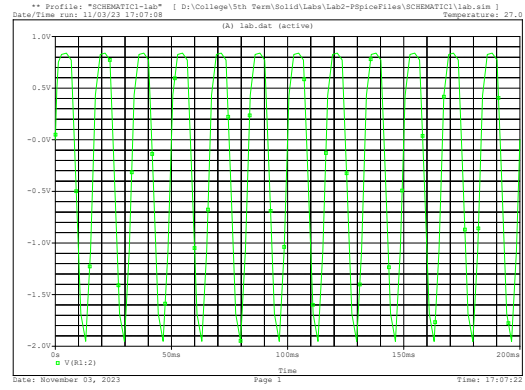


(b) $I_s = 10^{-10} A, N = 2$

Figure 3: N Change with Time Plots


1.2.1 Discussion

Analyze the results obtained we understand that more N value gives lower peak to peak voltage amount on the output as relation $V_D = NV_t \ln(\frac{I_d}{I_s} + 1)$ so N direct proportional with V_D .

1.3 Changing R_s with Time

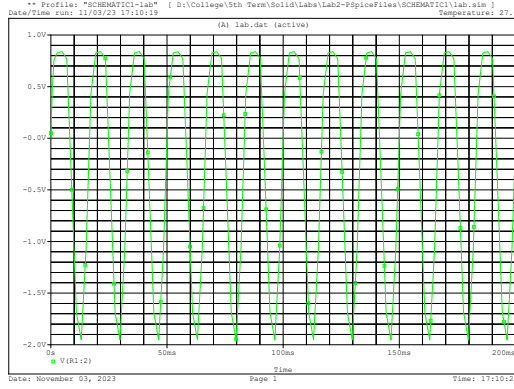

(a) $I_s = 10^{-10} A, N = 2, R_s = 0$

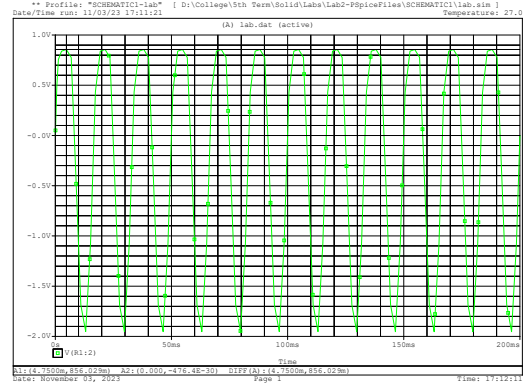


(b) $I_s = 10^{-10} A, N = 2, R_s = 16$

Figure 4: Changing R_s with Time Plots


1.3.1 Discussion

Analyze the results obtained we understand that more R_s value gives higher peak to peak voltage amount on the output as relation $V_D = R_s I_s + N V_t \ln(\frac{I_d}{I_s} + 1)$ so R_s direct proportional with V_D .

1.4 Changing R with Time

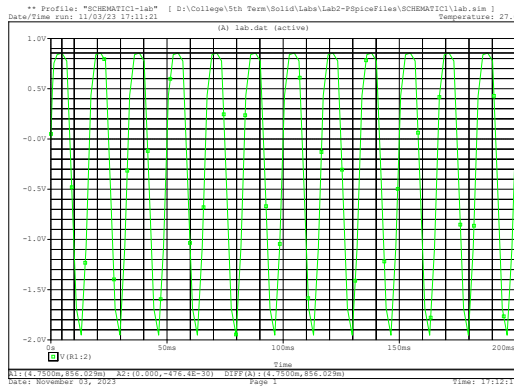

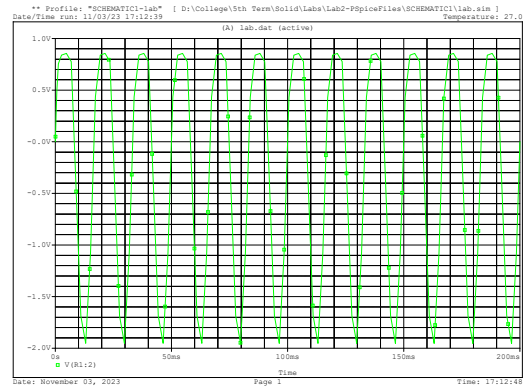(a) $I_s = 10^{-10} A, N = 2, R_s = 16, R = 1kohms$



(b) $I_s = 10^{-10} A, N = 2, R_s = 16, R = 50ohms$

Figure 5: Changing R with Time Plots

1.4.1 Discussion

Analyze the results obtained we understand that more R the voltage divider gives the resistance more voltage and make the R_s more neglected.



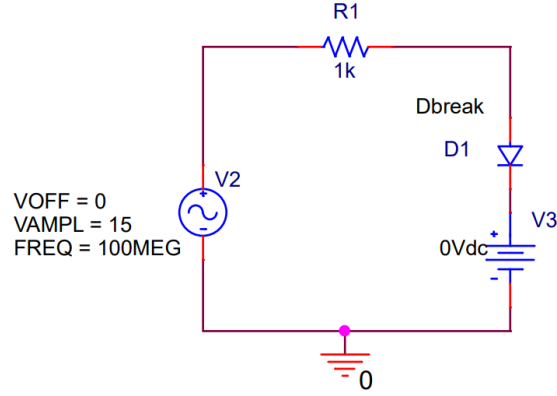


Figure 6: Modification

1.5 Changing TT with Time

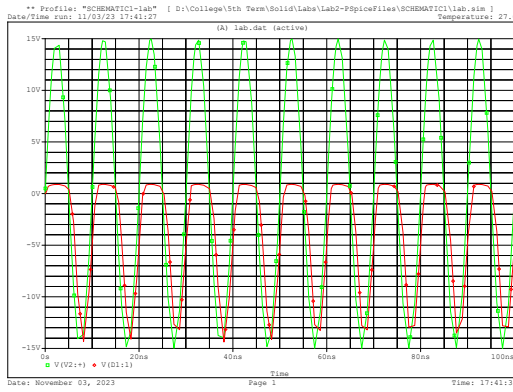

(a) $TT = 0$

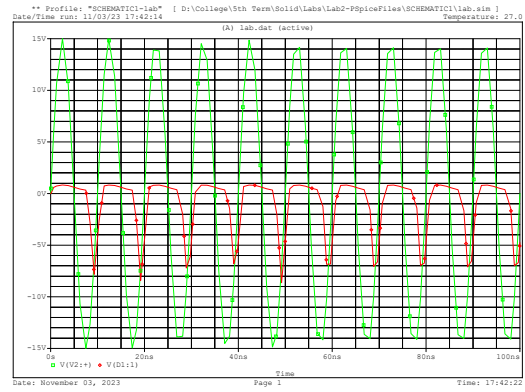

(b) $TT = 12ns$

$$I_s = 0.1pA, N = 1, R_s = 16, C_{Jo} = 2pF, M = 0.5, V_J = 0.75$$

Figure 7: Changing TT with Time Plots

1.5.1 Discussion

Due to relation $C_s = TT \frac{dI_D}{dV_{D_o}}$ as $C_D = C_d + C_s$ so it gives more output in inverse mode in $TT = 0$ as having more capacitance and fig. b has more oscillations.


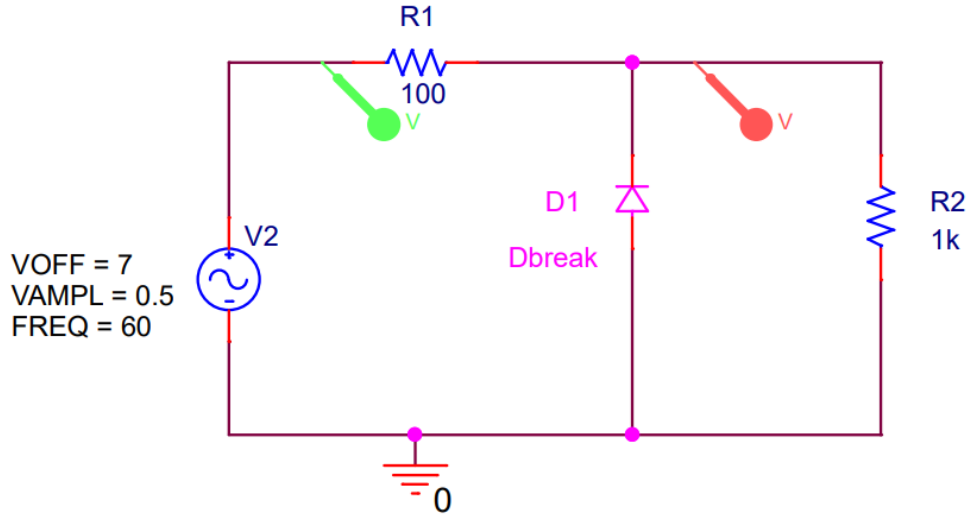



Figure 8: 2nd Circuit Simulation

2 2nd Circuit

2.1 BV Change with Time

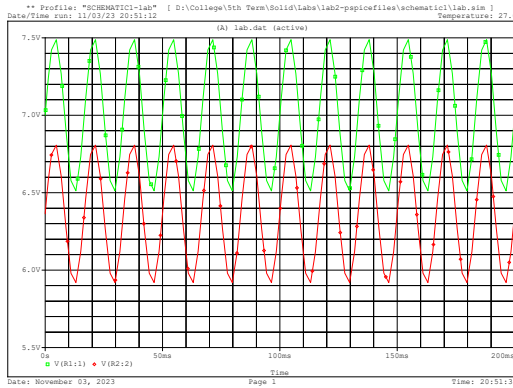

(a) $BV = \infty$

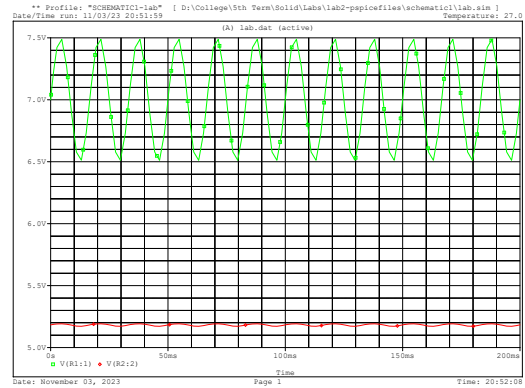


(b) $BV = 4.7$

Figure 9: BV Change with Time Plots

2.1.1 Discussion

Analyze the results obtained we understand that as BV tends to ∞ the peak to peak voltage amount tends to max on the output as relation $I_D = I_s(e^{\frac{BV+V_{D0}}{V_t}} - 1 + \frac{BV}{V_t})$.

2.2 R_s Change with BV and Time

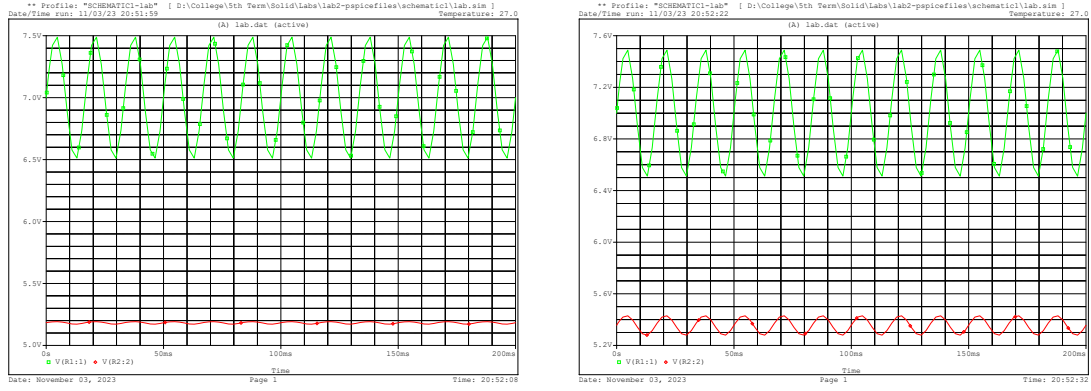

(a) $R_s = 0$

(b) $R_s = 16$

Figure 10: R_s Change with BV and Time Plots

2.2.1 Discussion

Analyze the results obtained we understand that more R_s value gives higher peak to peak voltage amount on the output as relation $I_D = I_s(e^{\frac{BV+V_{D0}}{V_t}} - 1 + \frac{BV}{V_t})$.

3 3rd Circuit



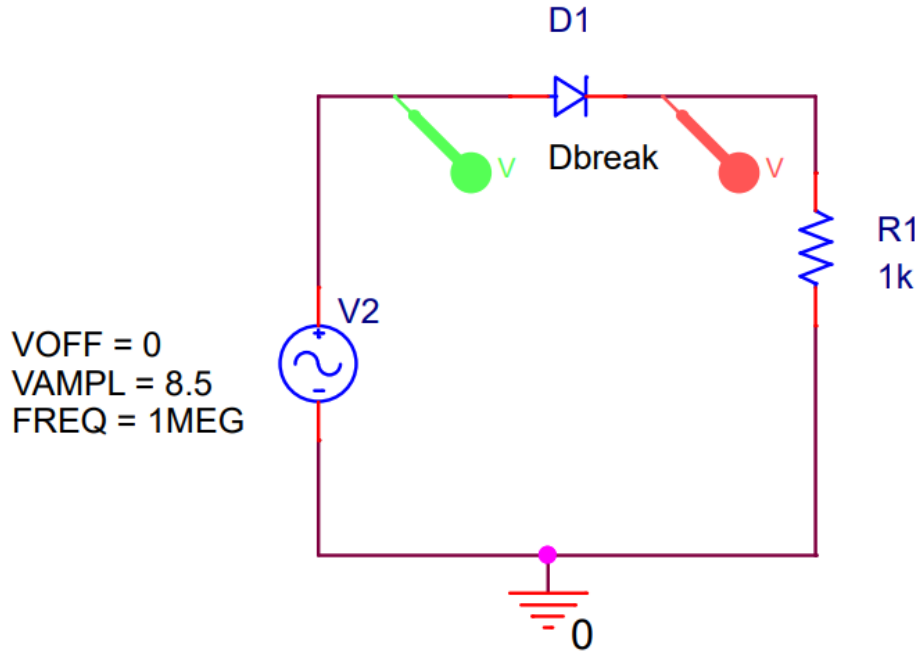


Figure 11: 3rd Circuit Simulation

3.1 Changing Parameters with Time

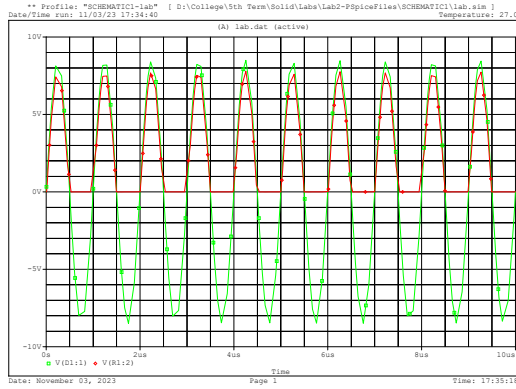

(a) Default

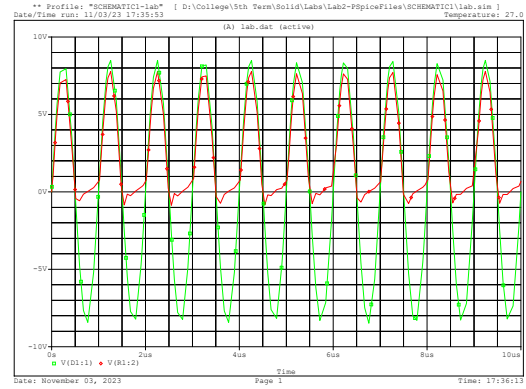

(b) $C_j = 20pF, M = 0.5, V_j = 0.75V$


Figure 12: Changing Parameters with Time

3.1.1 Discussion

The output in fig. a is have wave rectifier the output peak is less than input by 0.7V because of capacitance effect also we get here oscillations in the fig. b mode.


4 Appendix

<i>STATIC PARAMETERS</i>				
Symbol	Usual SPICE Keyword	Parameter Name	Typical Value/ Range	Unit
I_S	IS	Saturation current		A
n	N	Emission coefficient	1 – 2	
r_S	RS	Parasitic resistance		Ω
BV	BV	Breakdown voltage (positive number)		V
	IBV	Breakdown current (positive number)		A
Note: $IBV = IS \frac{BV}{V_t}$				
<i>STATIC DIODE MODEL</i>				

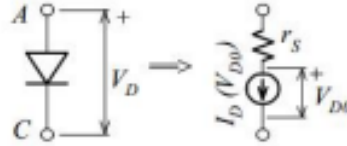

$$I_D(V_{D0}) = \begin{cases} IS (e^{V_{D0}/n V_t} - 1) + V_{D0} G_{MIN} & \text{if } V_{D0} > -BV \\ -IBV & \text{if } V_{D0} = -BV \\ -IS [e^{-(BV + V_{D0})/V_t} - 1 + \frac{BV}{V_t}] & \text{if } V_{D0} < -BV \end{cases}$$

<i>DYNAMIC PARAMETERS</i>				
Symbol	Usual SPICE Keyword	Parameter Name	Typical Value/ Range	Unit
$C_d(0)$	CJO	Zero-bias junction capacitance		F
V_{bi}	VJ	Built-in (junction) voltage	0.65 – 1.25	V
m	M	Grading coefficient	$\frac{1}{3} - \frac{1}{2}$	
τ_T	TT	Transit time		s
<i>LARGE-SIGNAL DIODE MODEL</i>				

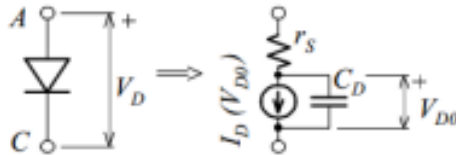

$I_D(V_{D0})$ is given in Table A.1

$$C_D = C_d + C_s$$

$$C_d = CJO \left(1 - \frac{V_{D0}}{VJ}\right)^{-M} \quad (\text{for } V_{D0} < 0.5VJ)$$

$$C_s = TT \frac{dI_D}{dV_{D0}}$$