

# Report of Lab 1:

## Static and Dynamic Diode Responses Using OrCAD

Islam Ibrahim - 21010247 - Section 5 - 2026  
Department of Electronics and Communication Engineering  
Alexandria University

### 1 Introduction

Before we delve into a detailed exploration of the dynamic and static aspects of diodes and their associated parameters, it's essential to acknowledge the significance of these characteristics in electronic circuits. Diodes are the unsung heroes of the electronics world, serving as key building blocks in a wide range of applications. Their ability to control the flow of current in one direction and their unique behaviors in response to dynamic changes in voltage and current make them indispensable. Understanding diode characteristics is the foundation upon which efficient circuit design, signal processing, and power management are built. In the following subsections, we will thoroughly examine the dynamic and static behaviors of diodes, shedding light on their applications and the critical parameters, such as capacitance, that underpin their functionality.

#### 1.1 Dynamic Diode Response

Diodes play a crucial role in dynamic circuit operations, especially in switching applications. In this subsection, we will explore how diodes respond to transient changes in voltage and current. This dynamic behavior is vital in various applications such as rectification, pulse shaping, and signal clamping.

##### 1.1.1 Diode Switching Characteristics

One of the fundamental dynamic aspects of diodes is their switching behavior. When subjected to abrupt changes in voltage, diodes experience a finite transition time between their on (conductive) and off (non-conductive) states. Understanding the switching characteristics of diodes is vital in applications like high-speed data transmission and power electronics.

##### 1.1.2 Recovery Time and Reverse Recovery Current

During the transition from the forward-biased to the reverse-biased state, diodes exhibit a phenomenon known as reverse recovery. This behavior leads to a delay in the diode's ability to block current in the reverse direction. The parameters associated with this dynamic response include the reverse recovery time  $t_{rr}$  and the reverse recovery current  $I_{rr}$ . These parameters are vital when designing circuits that require fast switching, as they can significantly impact circuit performance.

##### 1.1.3 Diode Capacitance

Capacitance in diodes is another critical dynamic parameter. Diodes inherently possess capacitance due to the nature of their construction. Two key capacitance parameters are the junction capacitance  $C_j$  and the diffusion capacitance  $C_d$ . These capacitances can influence high-frequency response and signal integrity in diode circuits. Engineers must consider these capacitance parameters when designing radio-frequency (RF) and microwave circuits, as well as high-speed digital systems.

## 1.2 Static Diode Response

In static conditions, diodes primarily operate as rectifiers, allowing current to flow in one direction while blocking it in the reverse direction. Understanding the static characteristics of diodes is essential for designing power supplies, signal conditioning circuits, and voltage regulation.

### 1.2.1 Voltage-Current Characteristics

Diodes have distinctive voltage-current  $VI$  characteristics, particularly when they are forward-biased and reverse-biased. In the forward-biased state, the diode has a low forward voltage drop and exhibits exponential behavior, while in the reverse-biased state, it acts as an open circuit, allowing minimal reverse leakage current.

### 1.2.2 Ideal vs. Practical Diodes

In real-world applications, diodes deviate from ideal behavior. Practical diodes exhibit characteristics like non-zero reverse leakage current, voltage drop in the forward-biased state, and dynamic resistance. Understanding the differences between ideal and practical diodes is essential for accurate circuit design and analysis.

In summary, dynamic and static responses of diodes are essential aspects of electronic circuit design. Diodes are not just static components used for rectification; they also exhibit dynamic behaviors that influence the performance of circuits in various applications. Moreover, parameters such as reverse recovery time, capacitance, and voltage-current characteristics must be considered to harness the full potential of diodes in different circuit scenarios. In the following sections of this report, we will discuss the experimental methods and results related to these dynamic and static characteristics of diodes using OrCAD.

## 2 Results on Resistance


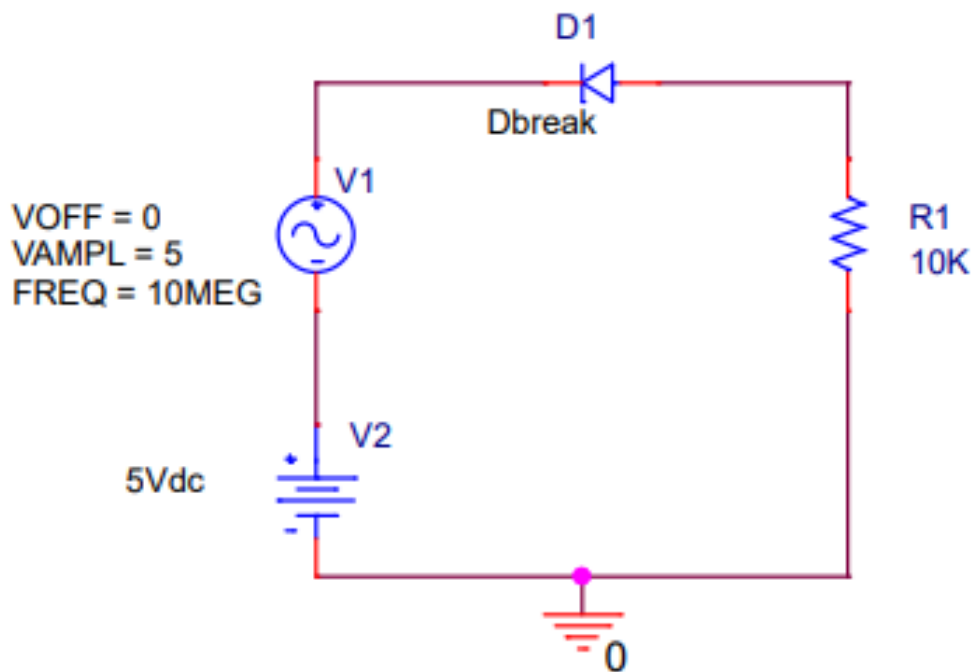



Figure 1: 1<sup>st</sup> Circuit Simulation

## 2.1 $C_{jo}$ Change with Time

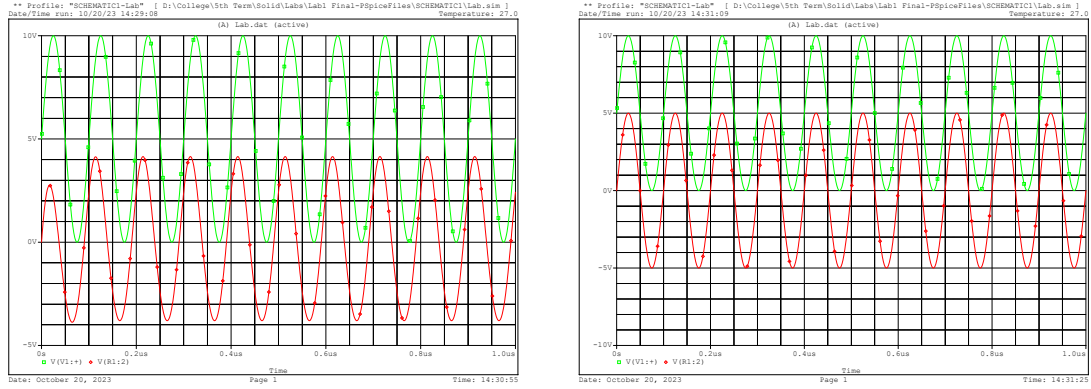

(a)  $C_{jo} = 5pF$

(b)  $C_{jo} = 15nF$

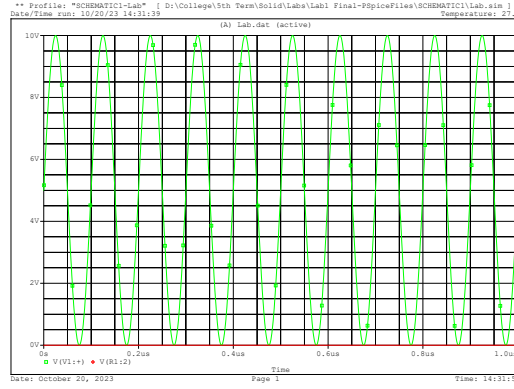


(c)  $C_{jo} = 10^{-20} F$

Figure 2:  $C_{jo}$  Change Simulation Plots


### 2.1.1 Discussion

Analyze the results obtained we understand that more  $C_{jo}$  value gives more impedance in the circuits as it make diode behave as capacitor in the reverse bias also when the  $C_{jo}$  reaches some tiny point it back to normal open circuit model.

## 2.2 Adding $M$ and $VJ$ with Time

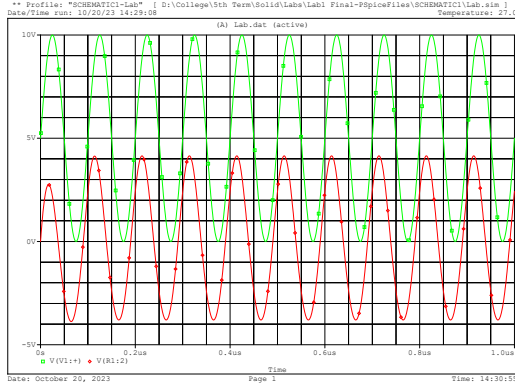

(a)  $C_{jo} = 5pF$

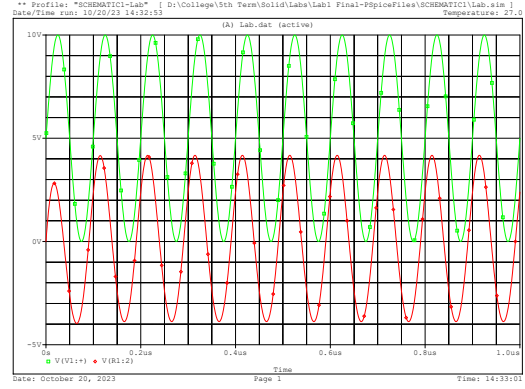


(b)  $C_{jo} = 5pF, M = 0.42, VJ = 0.75V$

Figure 3: Adding  $M$  and  $VJ$  Simulation Plots


### 2.2.1 Discussion

Due to Relation  $C_D = C_d + C_s$  as  $C_d = C_{Jo}(1 - \frac{V_{Do}}{VJ})^{-M}$  the result of the fig 3.b must have lower capacitance making circuit have higher impedance which make slight difference in the voltage on resistance.

## 2.3 Changing $V_{DC}$ with Time

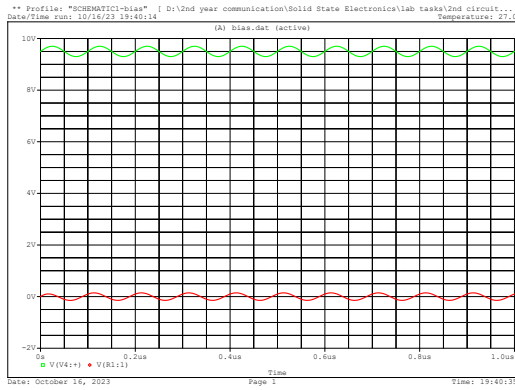

(a)  $C_{jo} = 5pF, V_{DC} = 9.5V$

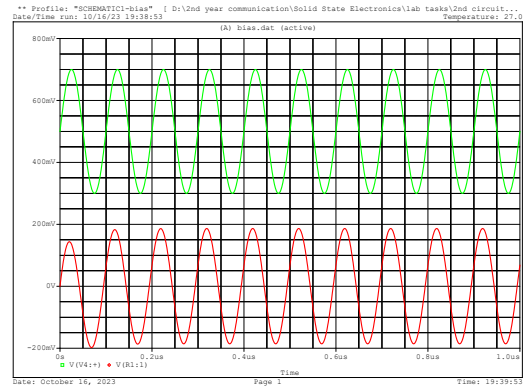


(b)  $C_{jo} = 5pF, V_{DC} = 0.5V$

Figure 4: Changing  $V_{DC}$  Simulation Plots

### 2.3.1 Discussion


Due to Relation  $C_j = A\sqrt{\frac{q\epsilon}{2(V_o - V)} \frac{N_d N_a}{N_d + N_a}}$  the results would have difference as inverse relation between  $C_j$  and  $V$ .
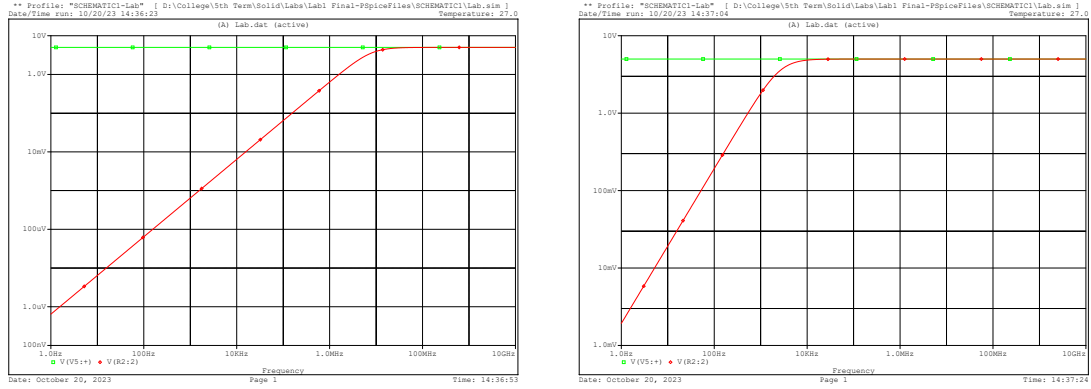
## 2.4 $C_{jo}$ Change with Frequency (log Scale)



(a)  $C_{jo} = 5pF$

(b)  $C_{jo} = 15nF$

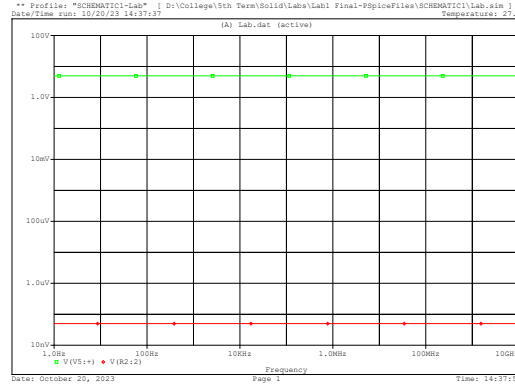


(c)  $C_{jo} = 10^{-20} F$

Figure 5:  $C_{jo}$  Change Simulation Plots

### 2.4.1 Discussion

Analyze the results obtained we understand that more  $C_{jo}$  value need higher frequency to reach short circuit state and at very small  $C_{jo}$  it will nearly always open circuit with all frequencies. Also, those have applications are called high pass filters.
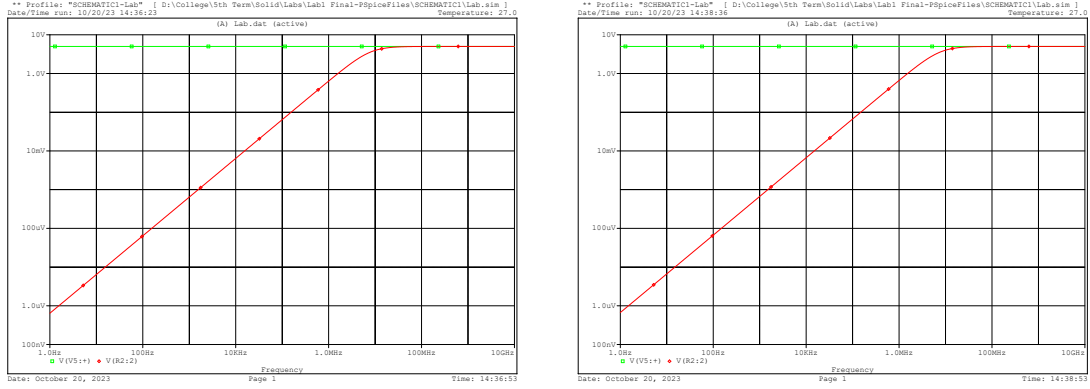
## 2.5 Adding $M$ and $VJ$ with Frequency (log Scale)



(a)  $C_{jo} = 5pF$


(b)  $C_{jo} = 5pF, M = 0.42, VJ = 0.75V$

Figure 6: Adding  $M$  and  $VJ$  Simulation Plots

### 2.5.1 Discussion

Due to Relation  $C_D = C_d + C_s$  as  $C_d = C_{Jo}(1 - \frac{V_{Do}}{V_J})^{-M}$  the result of the fig 6.b must have lower capacitance which response with lower frequencies to reach short circuit.
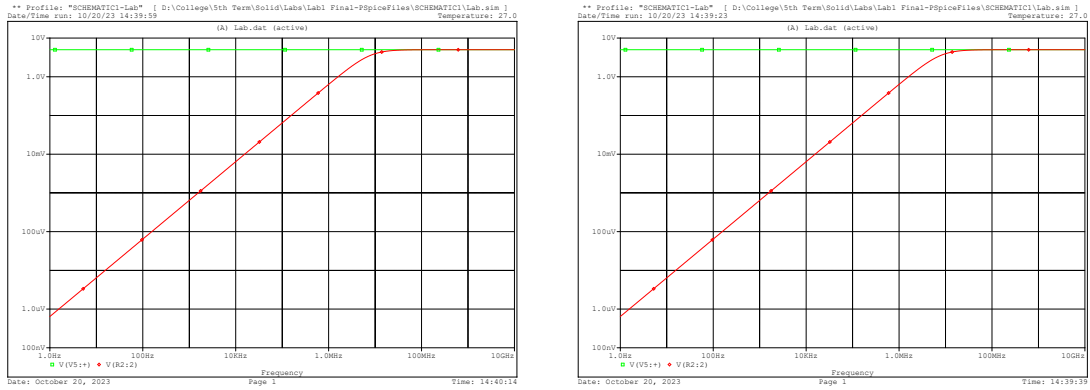
## 2.6 Changing $V_{DC}$ with Frequency (log Scale)



(a)  $C_{jo} = 5pF, V_{DC} = 9.5V$

(b)  $C_{jo} = 5pF, V_{DC} = 0.5V$

Figure 7: Changing  $V_{DC}$  Simulation Plots

### 2.6.1 Discussion

It will not make much difference as it was with Time because the DC does not have frequency change but it contribute in  $C_j$  so might have slight change.

### 3 Results on Diode



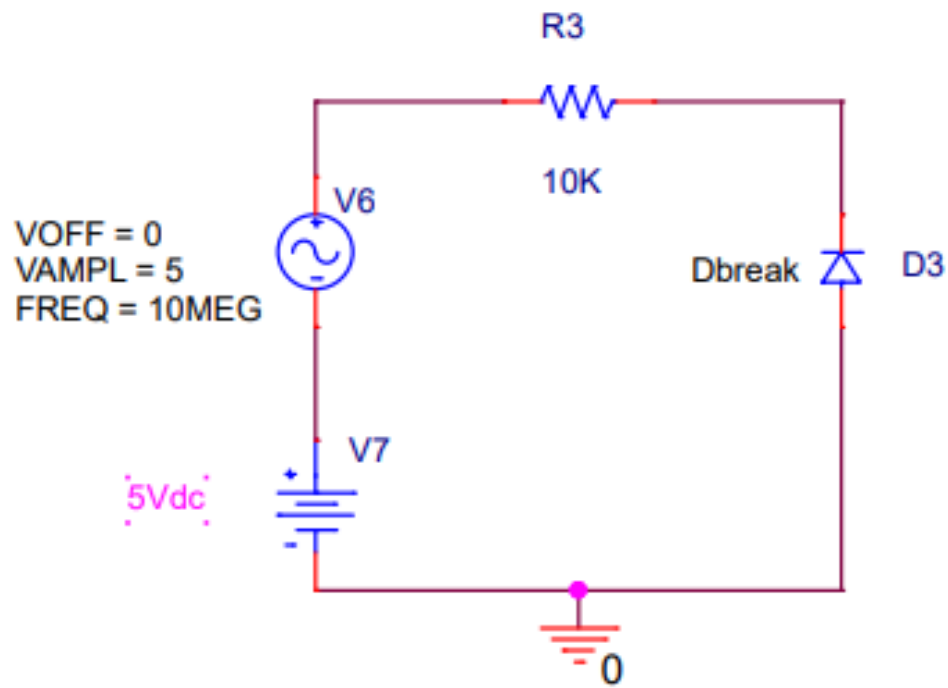


Figure 8: 2<sup>nd</sup> Circuit Simulation


### 3.1 $C_{jo}$ Change with Time

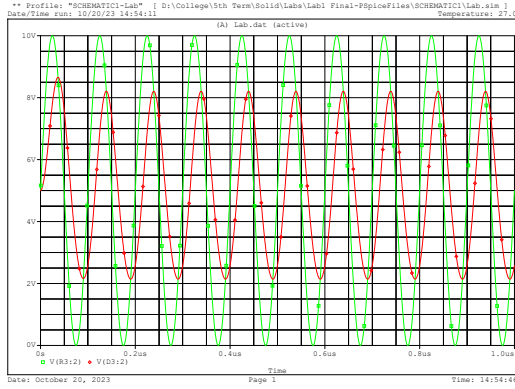

(a)  $C_{jo} = 5pF$

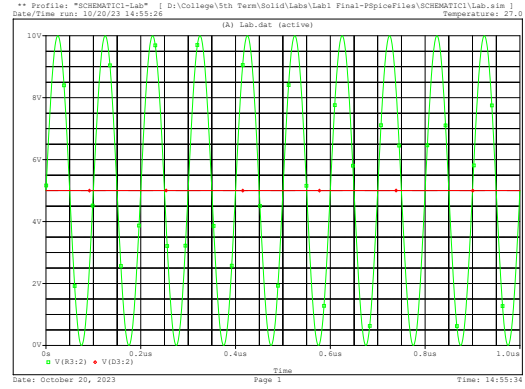

(b)  $C_{jo} = 15nF$

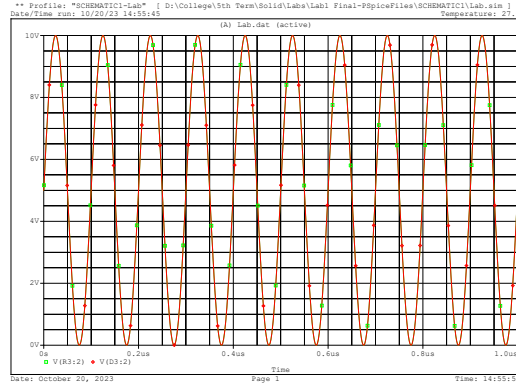

(c)  $C_{jo} = 10^{-20}F$


Figure 9:  $C_{jo}$  Change Simulation Plots

#### 3.1.1 Discussion

Analyze the results obtained we understand that more  $C_{jo}$  value gives more impedance in the circuits as it make diode behave as capacitor in the reverse bias also when the  $C_{jo}$  reaches some tiny point it back to normal open circuit model as fig 9.c, also in fig 9.b act as short circuit.



### 3.2 Adding $M$ and $VJ$ with Time

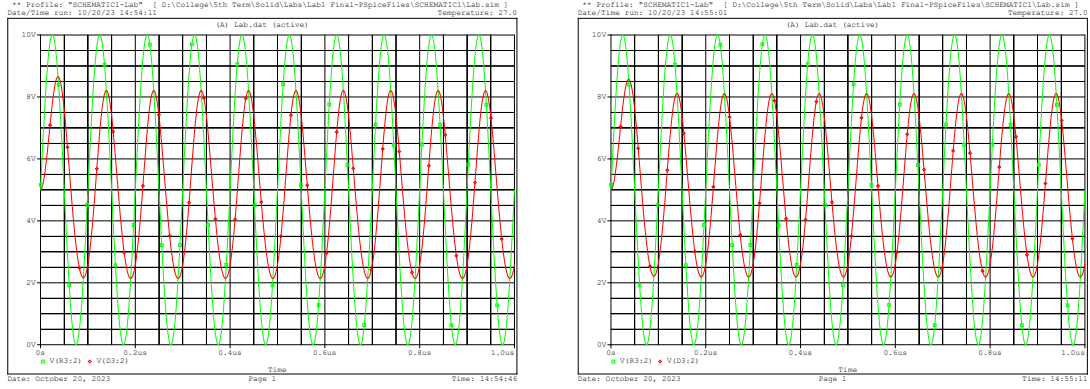

(a)  $C_{jo} = 5pF$


(b)  $C_{jo} = 5pF, M = 0.42, VJ = 0.75V$

Figure 10: Adding  $M$  and  $VJ$  Simulation Plots

#### 3.2.1 Discussion

Due to Relation  $C_D = C_d + C_s$  as  $C_d = C_{jo}(1 - \frac{V_{D2}}{V_J})^{-M}$  the result of the fig 10.b must have lower capacitance making circuit have higher impedance which make slight difference in the voltage on diode.

### 3.3 Changing $V_{DC}$ with Time

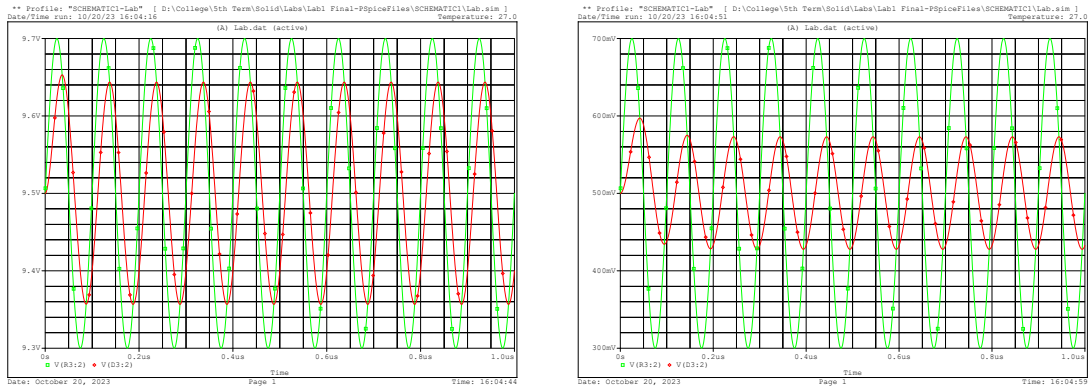

(a)  $C_{jo} = 5pF, V_{DC} = 9.5V$


(b)  $C_{jo} = 5pF, V_{DC} = 0.5V$

Figure 11: Changing  $V_{DC}$  Simulation Plots

#### 3.3.1 Discussion

Due to Relation  $C_j = A\sqrt{\frac{q\epsilon}{2(V_o - V)}} \frac{N_d N_a}{N_d + N_a}$  the results would have slight difference as inverse relation between  $C_j$  and  $V$ .

### 3.4 Parametric and DC

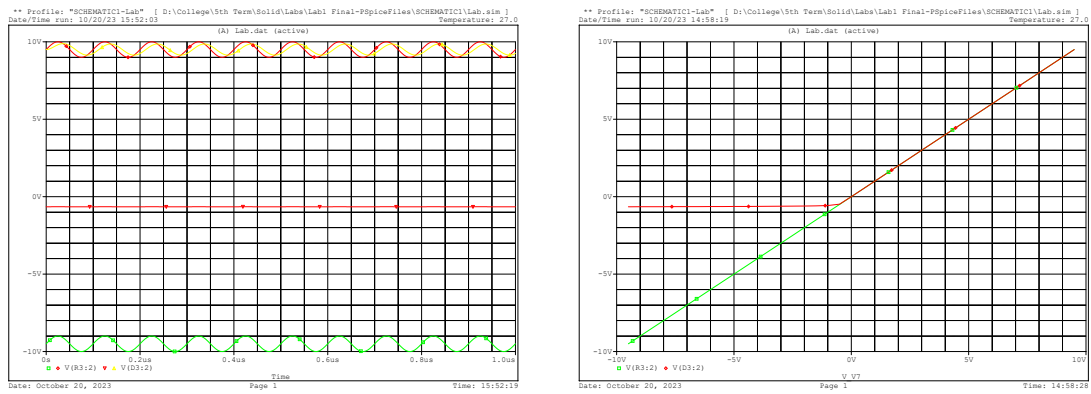

(a) Parametric Sweep


(b) DC Sweep

Figure 12: Changing  $V_{DC}$  Simulation Plots

#### 3.4.1 Discussion


Fig. 12.b shows that the diode remains forward bias as it constant value then become backward bias. As Fig. 12.a shows that when dc is +ve or -ve so when it negative it be short circuit as ideal model and when it positive it be backward bias and act as open circuit.
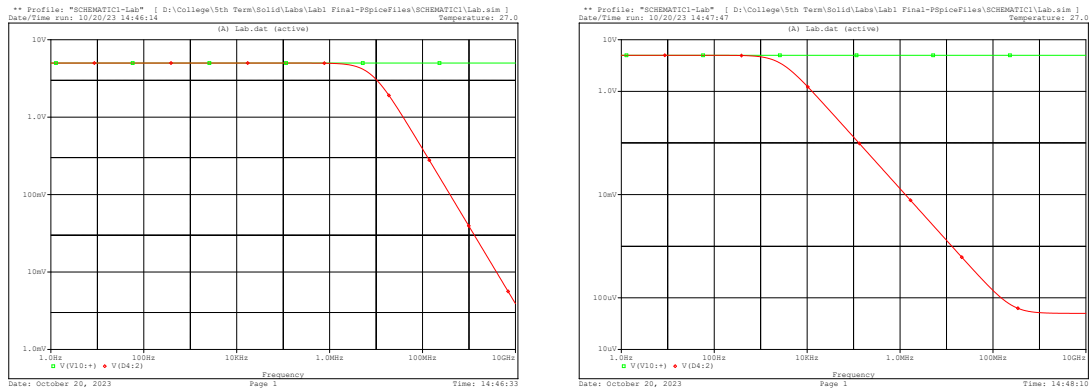
### 3.5 $C_{jo}$ Change with Frequency (log Scale)



(a)  $C_{jo} = 5pF$

(b)  $C_{jo} = 15nF$

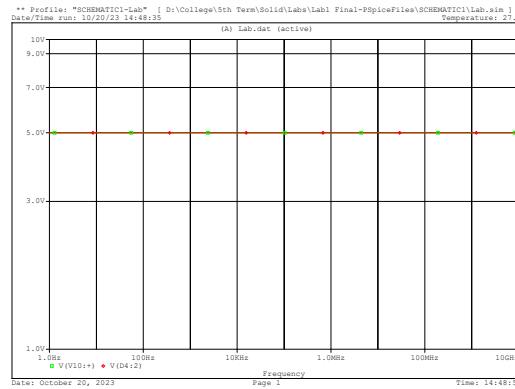


(c)  $C_{jo} = 10^{-20}F$

Figure 13:  $C_{jo}$  Change Simulation Plots

#### 3.5.1 Discussion

Analyze the results obtained we understand that more  $C_{jo}$  value need higher frequency to break the short circuit state and reach open circuit state and at very small  $C_{jo}$  it will nearly always open circuit with all frequencies. Also, those have applications called low pass filter.
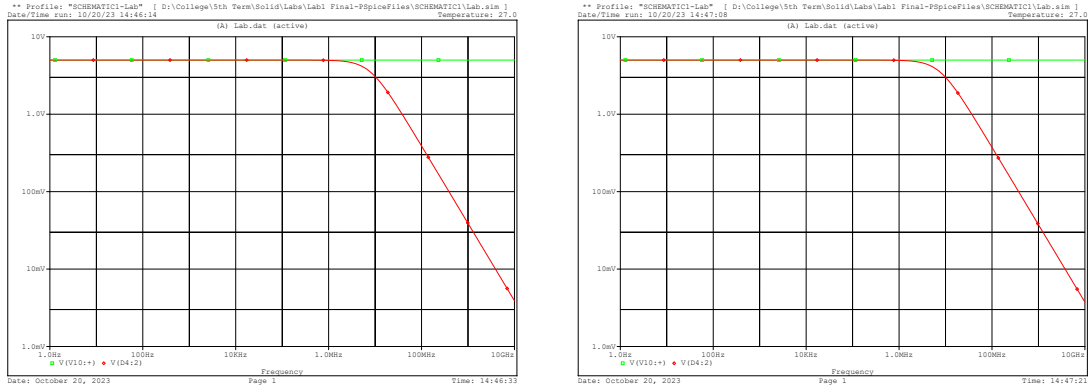
### 3.6 Adding $M$ and $VJ$ with Frequency (log Scale)



(a)  $C_{jo} = 5pF$


(b)  $C_{jo} = 5pF, M = 0.42, VJ = 0.75V$

Figure 14: Adding  $M$  and  $VJ$  Simulation Plots

#### 3.6.1 Discussion

Due to Relation  $C_D = C_d + C_s$  as  $C_d = C_{Jo}(1 - \frac{V_{DQ}}{V_J})^{-M}$  the result of the fig 14.b must have lower capacitance which response with lower frequencies to break short circuit state.
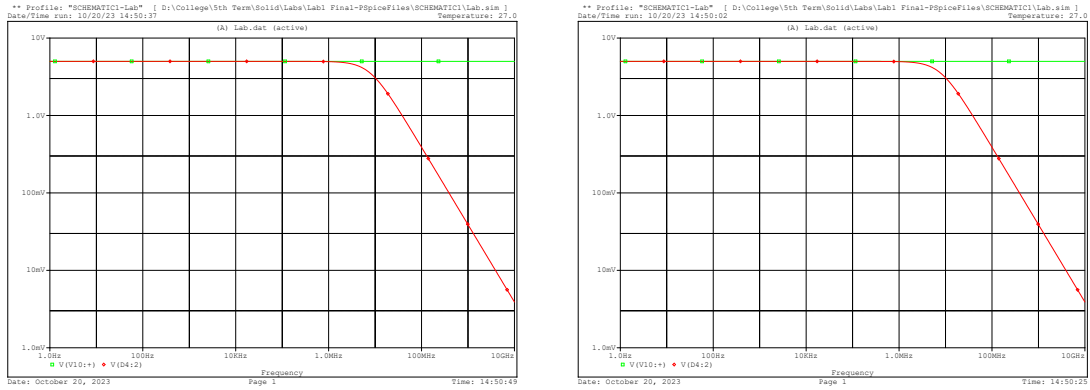
### 3.7 Changing $V_{DC}$ with Frequency (log Scale)



(a)  $C_{jo} = 5pF, V_{DC} = 9.5V$


(b)  $C_{jo} = 5pF, V_{DC} = 0.5V$

Figure 15: Changing  $V_{DC}$  Simulation Plots

#### 3.7.1 Discussion

It will not make much difference as it was with Time because the DC does not have frequency change but it contribute in  $C_j$  so might have slight change.

### 3.8 Parametric and DC

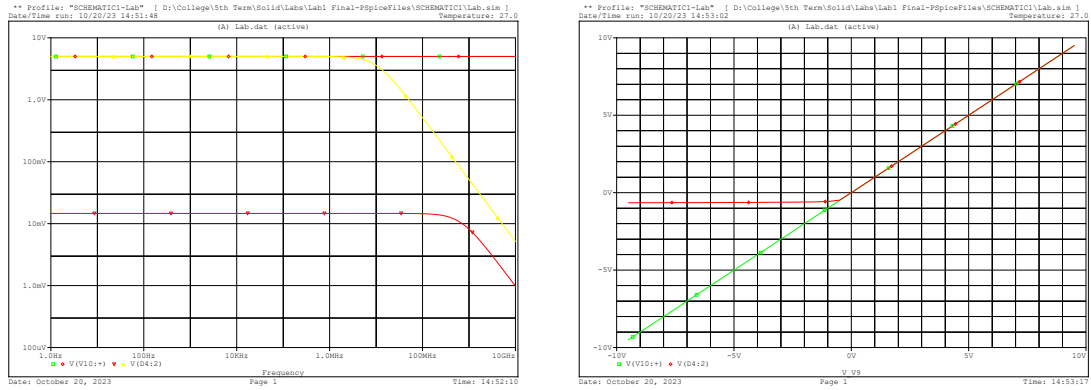

(a) Parametric Sweep (log Scale)

(b) DC Sweep


Figure 16: Changing  $V_{DC}$  Simulation Plots

#### 3.8.1 Discussion

Fig. 16.b shows that the diode remains forward bias as it constant value then become backward bias. Fig. 16.a Shows that voltage when it become negative it enlarge the  $C_j$  as it inverse proportional and operates on more frequency bandwidth before filtering.


## 4 Appendix

<i>STATIC PARAMETERS</i>				
Symbol	Usual SPICE Keyword	Parameter Name	Typical Value/ Range	Unit
$I_S$	IS	Saturation current		A
$n$	N	Emission coefficient	1 – 2	
$r_S$	RS	Parasitic resistance		$\Omega$
$BV$	BV	Breakdown voltage (positive number)		V
	IBV	Breakdown current (positive number)		A
Note: $IBV = IS \frac{BV}{V_t}$				
<i>STATIC DIODE MODEL</i>				

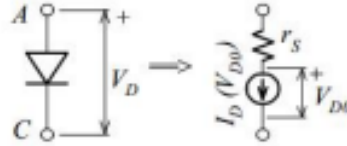

$$I_D(V_{D0}) = \begin{cases} IS (e^{V_{D0}/n V_t} - 1) + V_{D0} G_{MIN} & \text{if } V_{D0} > -BV \\ -IBV & \text{if } V_{D0} = -BV \\ -IS [e^{-(BV + V_{D0})/V_t} - 1 + \frac{BV}{V_t}] & \text{if } V_{D0} < -BV \end{cases}$$

<i>DYNAMIC PARAMETERS</i>				
Symbol	Usual SPICE Keyword	Parameter Name	Typical Value/ Range	Unit
$C_d(0)$	CJO	Zero-bias junction capacitance		F
$V_{bi}$	VJ	Built-in (junction) voltage	0.65 – 1.25	V
$m$	M	Grading coefficient	$\frac{1}{3} - \frac{1}{2}$	
$\tau_T$	TT	Transit time		s
<i>LARGE-SIGNAL DIODE MODEL</i>				

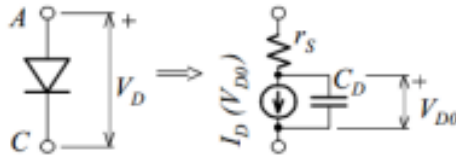

$I_D(V_{D0})$  is given in Table A.1

$$C_D = C_d + C_s$$

$$C_d = CJO \left(1 - \frac{V_{D0}}{VJ}\right)^{-M} \quad (\text{for } V_{D0} < 0.5VJ)$$

$$C_s = TT \frac{dI_D}{dV_{D0}}$$